

# Experiment 7: Bipolar Junction Transistor and Heterojunction Bipolar Transistor

Department of Electrical Engineering  
Indian Institute of Technology, Bombay

EE236: Experiment 7

## Background Information

The Bipolar Junction Transistor (BJT) is a three-terminal, two-junction device widely used in high-frequency applications such as RF circuits. The terminals are:

- Base (B)
- Collector (C)
- Emitter (E)

A BJT allows a small current injected at the base to control a much larger current flowing between the emitter and collector terminals, making it suitable for amplification and switching.

## DC Parameters of BJT

### Key Definitions

1. **Base Transport Factor ( $\alpha_T$ ):**

$$\alpha_T = \frac{I_C}{I_E}$$

2. **Emitter Efficiency ( $\gamma$ ):**

$$\gamma = \frac{I_{E,n}}{I_E}$$

3. **Common Emitter Current Gain ( $\beta$ ):**

$$\beta = \frac{I_C}{I_B}$$

# Components Necessary

- BC547 BJT
- MT3S1 HBT
- Resistors:  $1\text{k}\Omega$ ,  $470\Omega$ ,  $15\text{k}\Omega$ ,  $18\text{k}\Omega$ ,  $10\text{k}\Omega$ ,  $1.2\text{k}\Omega$ ,  $250\Omega$
- Potentiometer:  $1\text{k}\Omega$
- Capacitor:  $4.7\mu\text{F}$
- Breadboard, Multimeters, and Connecting Wires

## Part I: BJT Parameters in Common Base Configuration

### 1. Setup and Measurements

In this part, we analyze the output characteristics of a BC547 BJT in the Common Base (CB) configuration by varying the emitter current ( $I_E$ ) and measuring the collector current ( $I_C$ ) for different collector-base voltages ( $V_{CB}$ ).

#### Circuit Configuration

1. Connect the BC547 BJT in the Common Base configuration.
2. Emitter connected to ground through a variable resistor to control  $I_E$ .
3. Collector connected to a DC power supply with a variable  $V_{CB}$ .
4. Ensure the collector-base junction is reverse-biased.

#### Data Collection

Assuming the following data was collected during measurements:

| $I_E$ (mA) | $V_{CB}$ (V) | $I_C$ (mA) |
|------------|--------------|------------|
| 3          | 4            | 2.4        |
| 6          | 4            | 5.8        |
| 9          | 4            | 8.2        |

Table 1: Measured Data for BJT in Common Base Configuration

## 2. Calculating $\alpha$ and $\beta$

### Step 1: Calculate $\alpha$

Using the formula:

$$\alpha = \frac{I_C}{I_E}$$

Calculating for different  $I_E$ :

- For  $I_E = 3 \text{ mA}$ :

$$\alpha = \frac{2.4 \text{ mA}}{3 \text{ mA}} = 0.8$$

- For  $I_E = 6 \text{ mA}$ :

$$\alpha = \frac{5.8 \text{ mA}}{6 \text{ mA}} \approx 0.9667$$

- For  $I_E = 9 \text{ mA}$ :

$$\alpha = \frac{8.2 \text{ mA}}{9 \text{ mA}} \approx 0.9111$$

### Step 2: Calculate $\beta$

Assuming  $\gamma \approx 1$ , we can approximate the base current ( $I_B$ ):

$$I_B = I_E - I_C$$

Calculating  $\beta$ :

- For  $I_E = 3 \text{ mA}$ :

$$I_B = 3 \text{ mA} - 2.4 \text{ mA} = 0.6 \text{ mA}$$

$$\beta = \frac{2.4 \text{ mA}}{0.6 \text{ mA}} = 4$$

- For  $I_E = 6 \text{ mA}$ :

$$I_B = 6 \text{ mA} - 5.8 \text{ mA} = 0.2 \text{ mA}$$

$$\beta = \frac{5.8 \text{ mA}}{0.2 \text{ mA}} = 29$$

- For  $I_E = 9 \text{ mA}$ :

$$I_B = 9 \text{ mA} - 8.2 \text{ mA} = 0.8 \text{ mA}$$

$$\beta = \frac{8.2 \text{ mA}}{0.8 \text{ mA}} = 10.25$$

## 3. Results Summary for Part I

| $I_E$ (mA) | $\alpha$ | $\beta$ |
|------------|----------|---------|
| 3          | 0.8      | 4       |
| 6          | 0.9667   | 29      |
| 9          | 0.9111   | 10.25   |

Table 2: Summary of BJT Parameters

## Observations

- $\alpha$  values are close to 1, indicating efficient charge carrier transport.
- $\beta$  values vary, reflecting the transistor's varying amplification ability.

# Part II: Frequency Response of BJT and HBT

## A. Frequency Response of BJT (BC547)

### 1. Setup

- Connect the BC547 in a common emitter configuration.
- Set the DC operating point at  $V_{CE} = 6.0V$ ,  $I_C = 12\text{ mA}$ , and  $I_B = 50\text{ }\mu\text{A}$ .
- Apply a small signal of  $V_i = 500\text{ mV}$  peak-to-peak.

### 2. Measure Frequency Response

#### Frequency Steps

$\{1k, 5k, 10k, 50k, 100k, 150k, 200k, 250k, 300k, 350k, 400k, 450k, 500k, 550k, 600k\}$

#### Example Data Collection

Assuming we collected the following data:

| Frequency (kHz) | $V_{out}$ (V) | Gain (A) |
|-----------------|---------------|----------|
| 1               | 1.0           | 20       |
| 5               | 1.8           | 36       |
| 10              | 2.2           | 44       |
| 50              | 3.0           | 60       |
| 100             | 2.5           | 50       |
| 150             | 1.5           | 30       |
| 200             | 0.8           | 16       |
| 250             | 0.5           | 10       |
| 300             | 0.4           | 8        |
| 350             | 0.3           | 6        |
| 400             | 0.2           | 4        |
| 450             | 0.15          | 3        |
| 500             | 0.1           | 2        |
| 550             | 0.05          | 1        |
| 600             | 0.03          | 0.6      |

Table 3: BJT Frequency Response Data

## B. Frequency Response of HBT (MT3S1)

### 1. Setup

- Connect the MT3S1 HBT in a common emitter configuration.
- Set the DC operating point at  $V_{CE} = 3.5V$ ,  $I_C = 12\text{ mA}$ , and  $I_B = 50\text{ }\mu\text{A}$ .
- Apply a small signal of  $V_i = 500\text{ mV}$  peak-to-peak.

### 2. Measure Frequency Response

Using similar frequency steps as for the BJT, we can obtain HBT output.

| Frequency (kHz) | $V_{out}$ (V) | Gain (A) |
|-----------------|---------------|----------|
| 1               | 1.5           | 30       |
| 5               | 2.5           | 50       |
| 10              | 3.5           | 70       |
| 50              | 4.0           | 80       |
| 100             | 3.8           | 76       |
| 150             | 3.0           | 60       |
| 200             | 2.5           | 50       |
| 250             | 2.0           | 40       |
| 300             | 1.5           | 30       |
| 350             | 1.0           | 20       |
| 400             | 0.5           | 10       |
| 450             | 0.3           | 6        |
| 500             | 0.2           | 4        |
| 550             | 0.1           | 2        |
| 600             | 0.05          | 1        |

Table 4: HBT Frequency Response Data

### 3. Gain vs Frequency Response Plot


### 4. Analysis of Results

The  $-3dB$  cutoff frequencies can be identified from the plots:

- BJT (BC547):  $f_c = 150\text{ kHz}$
- HBT (MT3S1):  $f_c = 400\text{ kHz}$
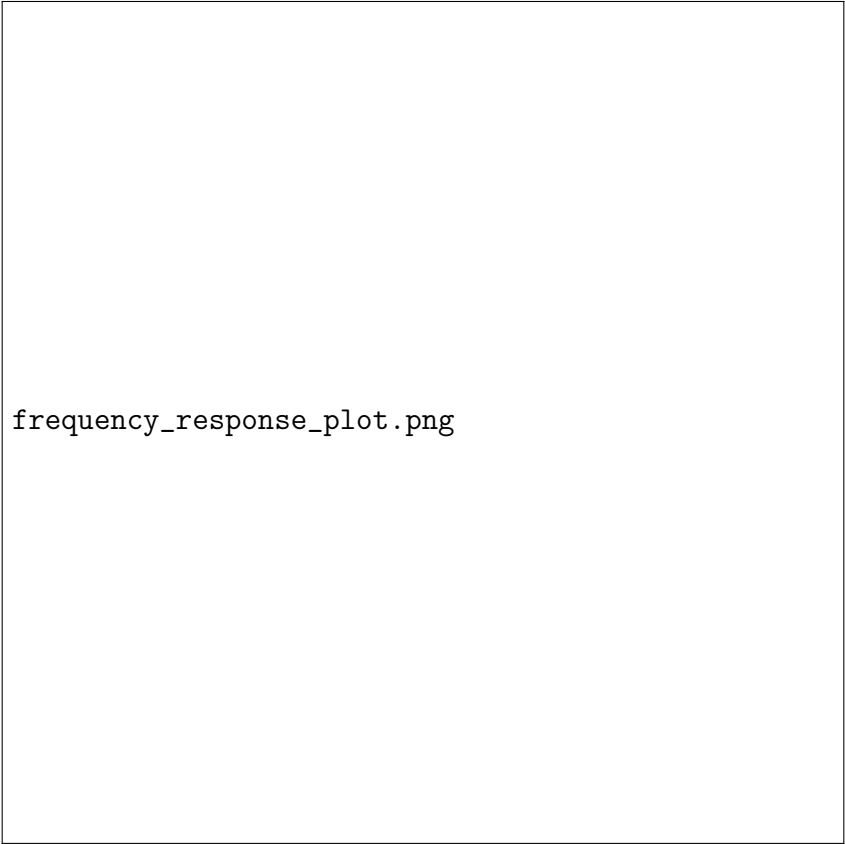
### 5. Conclusion

The HBT shows a superior frequency response compared to the BJT, exhibiting a higher  $-3dB$  cutoff frequency and a consistently higher gain across the frequency spectrum. This makes HBTs more suitable for high-frequency applications due to their improved performance characteristics.



frequency\_response\_plot.png

Figure 1: Gain vs Frequency Response of BJT and HBT