

EE236: Experiment No. 9

N Channel MOSFET Characteristics

Jatin Kumar, 22B3922

October 10, 2024

1 Overview of the experiment

1.1 Aim of the experiment

The aim of the experiment is to measure output and transfer characteristics of a NMOS transistor. To also investigate the effect of body bias on the characteristics of the NMOS.

1.2 Lab Experiment

1.3 Part 1 - Transfer Characteristics (Linear)

1.3.1 Circuit Used for Part 1

1.3.2 Readings Obtained

V _{GS} (in V)	I _D (in mA)
1.21	0.001
1.275	0.003
1.316	0.006
1.369	0.011
1.62	0.052
1.67	0.067
1.68	0.070
1.74	0.084
1.77	0.094
1.83	0.115
1.93	0.145
2.10	0.178
2.15	0.187
2.18	0.197
2.24	0.205
2.36	0.221
2.42	0.231
2.48	0.245
2.51	0.252
2.57	0.267
2.84	0.320
2.94	0.330
3.01	0.334

Table 1: $V_{DS} = 0.2V$, Linear Region Readings

1.3.3 Plot Obtained

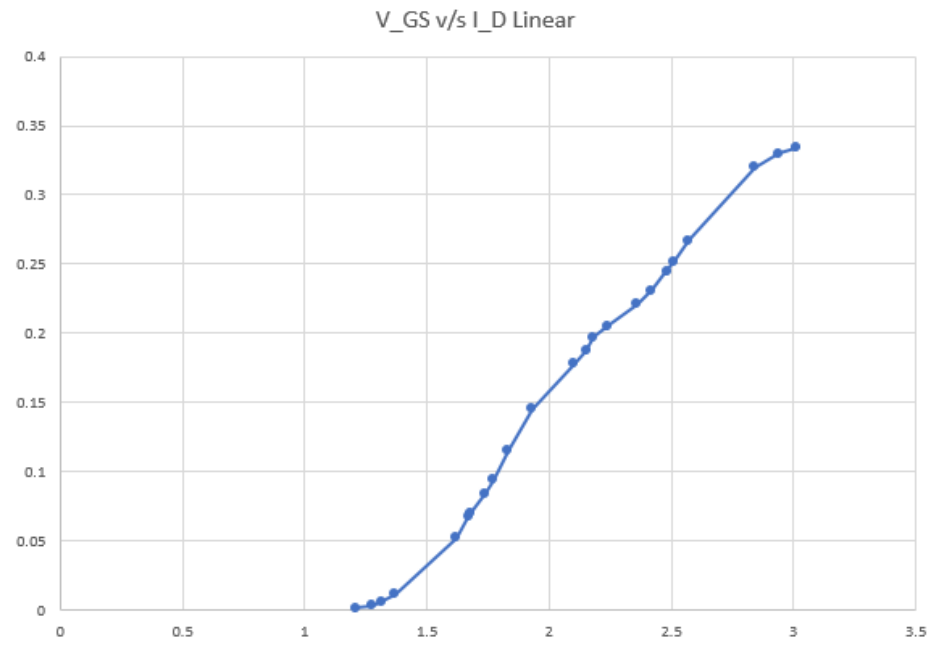


Figure 1: Transfer Characteristics Linear Plot

1.4 Part 1 - Transfer Characteristics (Saturation)

1.4.1 Circuit Used for Part 1

1.4.2 Readings Obtained

V _{GS} (in V)	I _D (in mA)
1.135	0
1.365	0.015
1.38	0.024
1.442	0.028
1.495	0.034
1.545	0.041
1.584	0.054
1.615	0.064
1.67	0.081
1.715	0.105
1.762	0.124
1.78	0.132
1.795	0.135
1.81	0.145
1.834	0.160
1.854	0.162
1.882	0.174
1.915	0.198
1.94	0.215
1.979	0.235
2.01	0.265
2.21	0.412
2.31	0.481
2.39	0.564
2.49	0.645
2.61	0.762
2.71	0.862
2.82	0.971
2.9	1.054
3.00	1.145

Table 2: $V_{DS} = 3V$, Saturation Region Readings

1.4.3 Plot Obtained

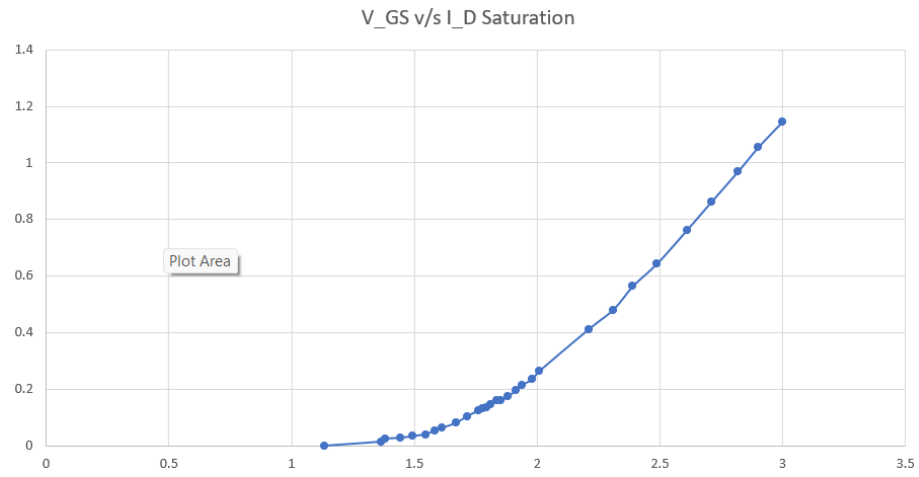


Figure 2: Transfer Characteristics Saturation Plot

1.5 Part 2 - Drain Characteristics

1.5.1 Circuit Used for Part 2

1.5.2 Readings Obtained

V_DS (in V)	I_D (mA)				
0.02	0.008				
0.03	0.014				
0.10	0.052				
0.20	0.096	V_DS (in V)	I_D (mA)	V_DS (in V)	I_D (mA)
0.26	0.112	0.25	0.295	0.25	0.540
0.30	0.118	0.45	0.473	0.45	0.930
0.34	0.122	0.65	0.589	0.65	1.260
0.39	0.125	0.85	0.646	0.85	1.540
0.44	0.127	1.05	0.664	1.05	1.740
0.50	0.128	1.25	0.670	1.25	1.880
0.56	0.128	1.45	0.673	1.45	1.990
0.68	0.129	1.65	0.675	1.65	2.030
0.78	0.130	1.85	0.677	1.85	2.050
0.90	0.130	2.05	0.678	2.05	2.070
1.10	0.131	2.25	0.680	2.25	2.080
1.30	0.131	2.45	0.681	2.45	2.080
1.50	0.132	2.65	0.682	2.65	2.080
1.70	0.132	2.85	0.683	2.85	2.080
1.90	0.132	3.05	0.684	3.05	2.090
2.10	0.132	3.25	0.685	3.25	2.090
2.40	0.133	3.45	0.686	3.45	2.100
2.70	0.134	3.65	0.686	3.65	2.100
3.00	0.134	3.85	0.687	3.85	2.100
3.30	0.135	4.05	0.688	4.05	2.110
3.60	0.135	4.25	0.688	4.25	2.110
3.90	0.135	4.45	0.689	4.45	2.110
4.20	0.136	4.65	0.690	4.65	2.110
4.50	0.136	4.85	0.691	4.85	2.120
4.80	0.137	5.00	0.691	5.00	2.120
5.00	0.137				

Table 4: V_{GS} = 2.5V

Table 5: V_{GS} = 3.5V

Table 3: V_{GS} = 1.5V

1.5.3 Plot Obtained

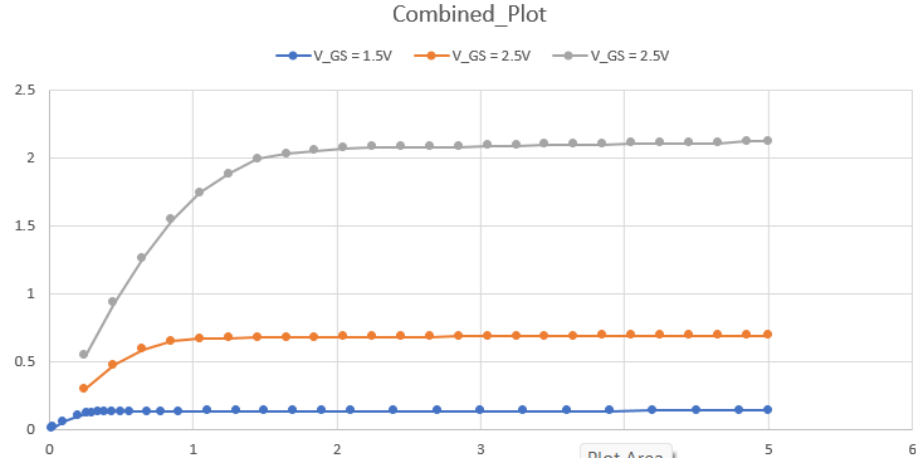


Figure 3: Combined Drain Characteristics plot

1.6 Part 3 - Body Effect

1.6.1 Circuit Used for Part 3

1.6.2 Readings Obtained

V_GS (in V)	I_D (mA)				
V_GS (in V)	I_D (mA)	V_GS (in V)	I_D (mA)	V_GS (in V)	I_D (mA)
2.24	0	3.04	0	3.71	0
2.28	0.002	3.12	0.002	3.75	0.001
2.60	0.040	3.41	0.052	4.08	0.047
2.83	0.110	3.54	0.105	4.16	0.065
3.02	0.170	3.81	0.145	4.25	0.088
3.23	0.210	4.04	0.203	4.35	0.112
3.44	0.264	4.32	0.271	4.51	0.152
3.68	0.307	4.43	0.310	4.59	0.170
4.01	0.384	4.77	0.351	4.66	0.192
4.15	0.402	4.95	0.394	4.78	0.215
4.54	0.485			4.85	0.235
4.75	0.510			4.95	0.254
4.95	0.534				

Table 7: $V_{SB} = 2V$

Table 6: $V_{SB} = 1V$

Table 8: $V_{SB} = 3V$

1.6.3 Plot Obtained

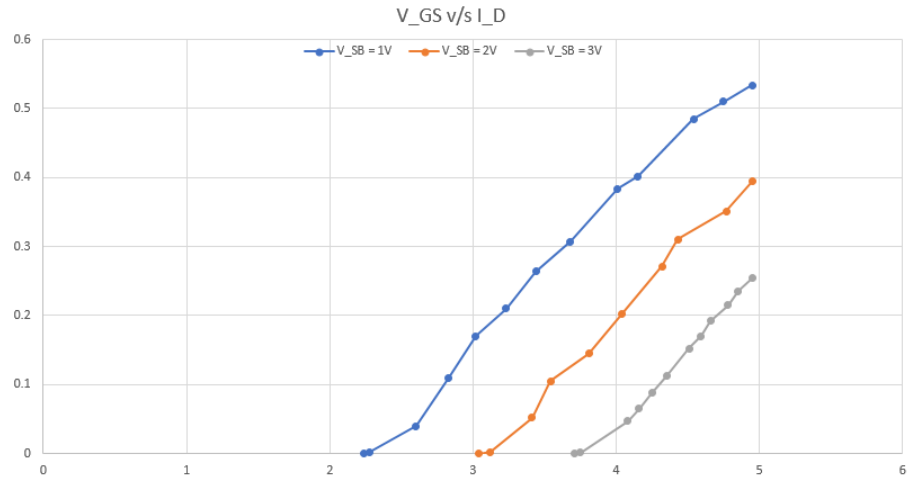


Figure 4: Combined Body Effect Plot

1.6.4 V_SB vs V_T Readings

V_SB (in V)	V_T (in V)
0	1.22
1	2.26
2	3.05
3	3.70

Table 9: V_SB vs V_T Readings

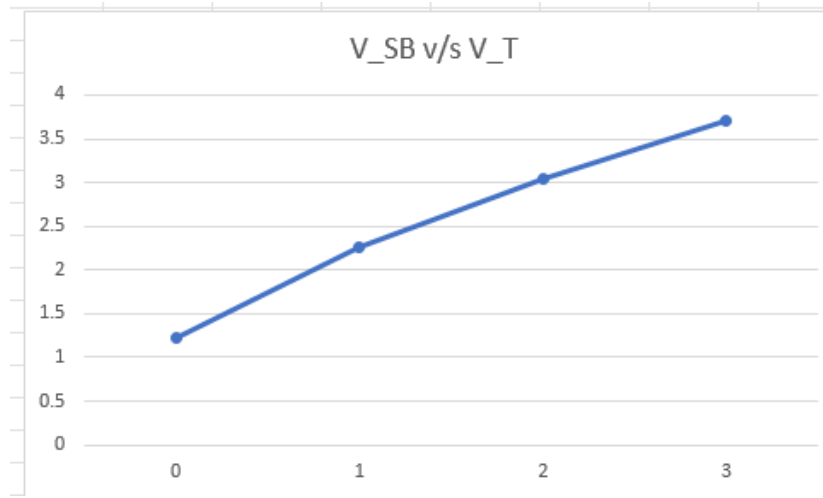


Figure 5: Plot of V_{SB} vs V_T

2 Calculations

2.1 Part 1

For Linear Region, $I_d = K(V_{sg} - V_t - 0.1)$ as $V_{sd} = 0.2V$. The value of K was approximated from the graph for the linear area region as $29.56e-6$ A/V. The V_t is calculated as $V_{sg} - I_d/K - 0.1$, for $V_{sg} = 1.8V$ was obtained as 0.123 V.

The value of g_m is nothing but the slope, which is K which we got as $29.56\mu A/V$.